

## Project: Single Cycle RISC-V

### 1. Introduction

in the area of Computer Architecture, it was originally designed to support research and education, for academic and industrial applications RISC-V instruction set architecture (ISA) is now set to become a standard free and open architecture. For the success and adoption of RISC-V, 32-bit, 64-bit and 128-bit address spaces support by RISC-V.

A minimal set of instructions adequate to provide a reasonable target for assemblers, linkers, compilers and operating systems, the ISA is separated into a small base integer ISA. The set of compatible tool chains which includes the above Suits, provided by RISC-V foundation.

In this architecture it provides the following set of **RV32I instructions**:

**R-Type: add, sub, and, or**

**I-Type: addi, andi, ori, lw, jalr**

**B-Type: beq, bne**

**J-Type: jal**

**S-Type: sw**

You can add more instructions by modifying the architecture in terms of muxes and the width of control lines.

To calculate the execution time:

$$T_{exec} = \text{instructions} * CPI \left( \frac{\text{cycle}}{\text{instruction}} \right) * T_c \left( \frac{\text{seconds}}{\text{cycle}} \right)$$

In our example we testcase we have #instructions = 16 instructions , CPI = 1 (single cycle),  $T_c$  is calculated by evaluate the critical path for the longest instruction which is lw instruction.


$$T_c = t_{pcqpc} + 2t_{mem} + t_{RFread} + t_{alu} + t_{mux} + t_{RFsetup}$$

$$T_c = 10 + 2 * 100 + 50 + 50 + 10 + 10 = 330 \text{ ps}$$


We can now evaluate the minimum execution time for our single-cycle RISC-V:

$$T_{exec} = 16 * 1 * 330 = 5280 \text{ ps} = 5.28 \text{ ns}$$


## 2.block diagram

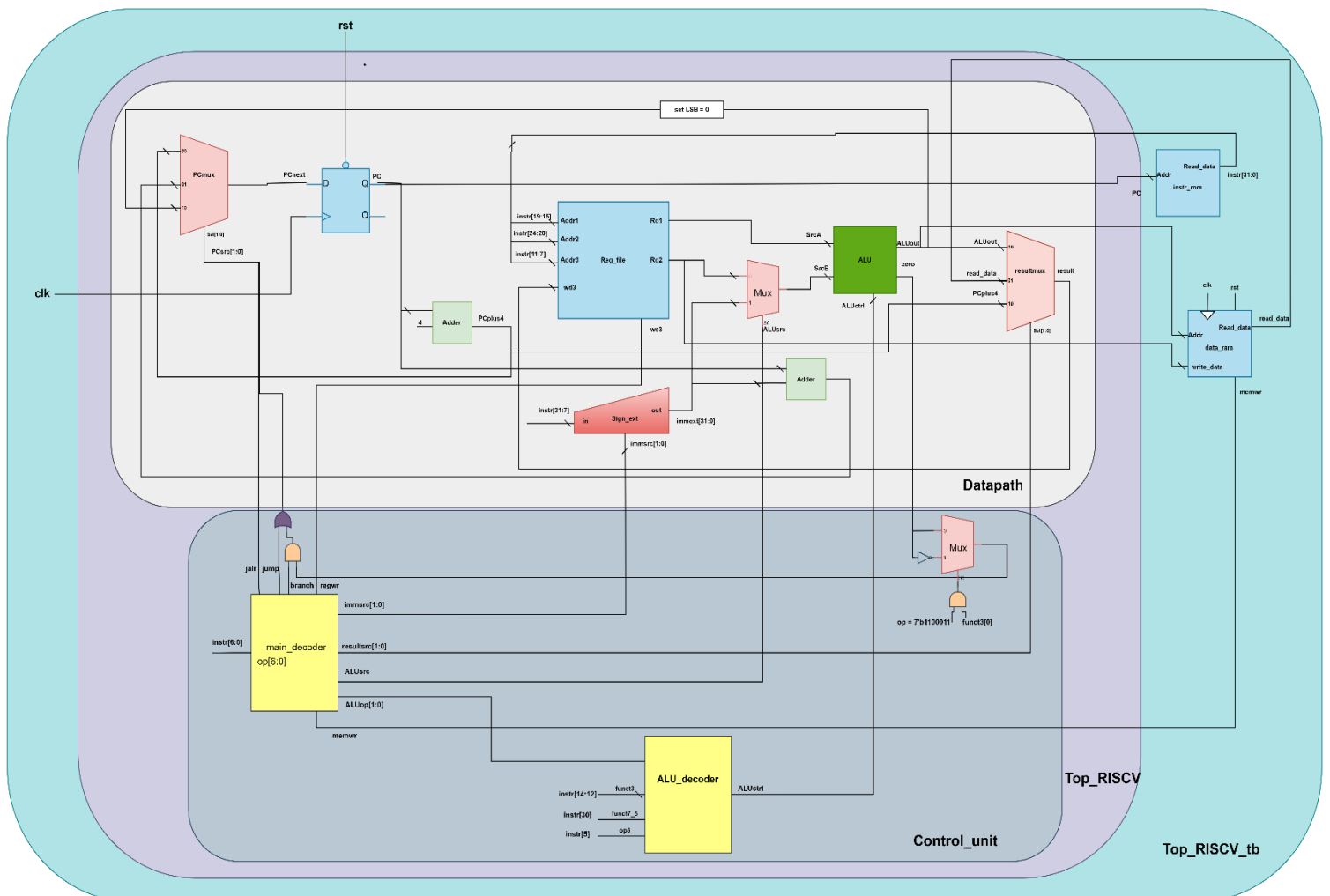

## 2.1 control unit

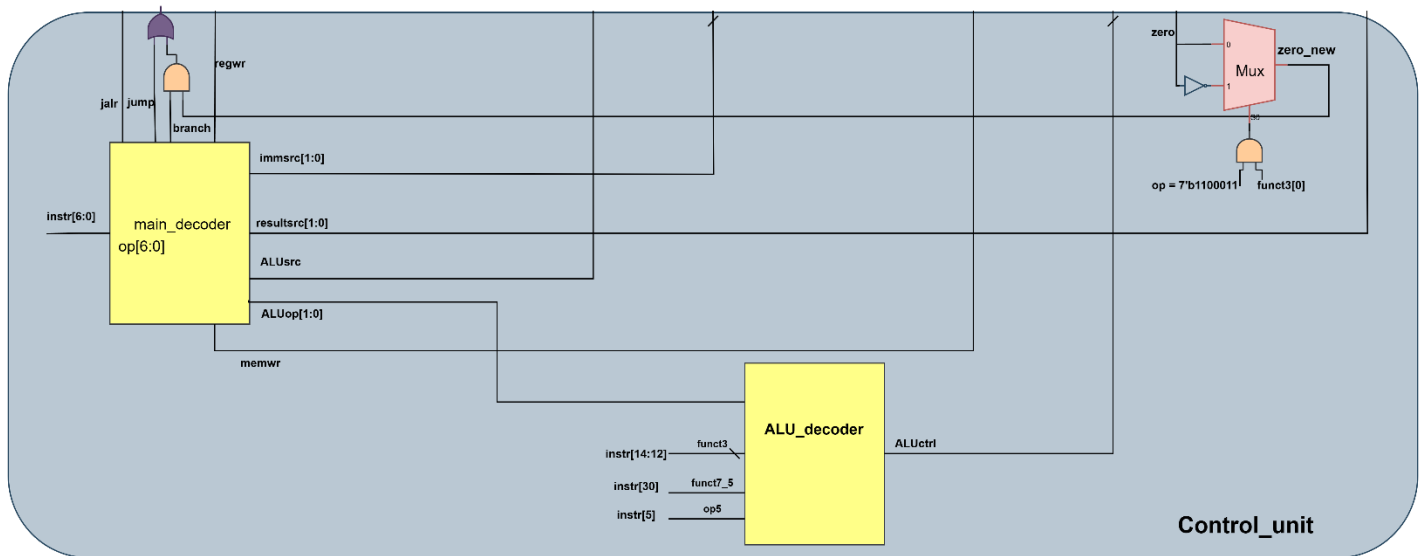

## 2.2 data path

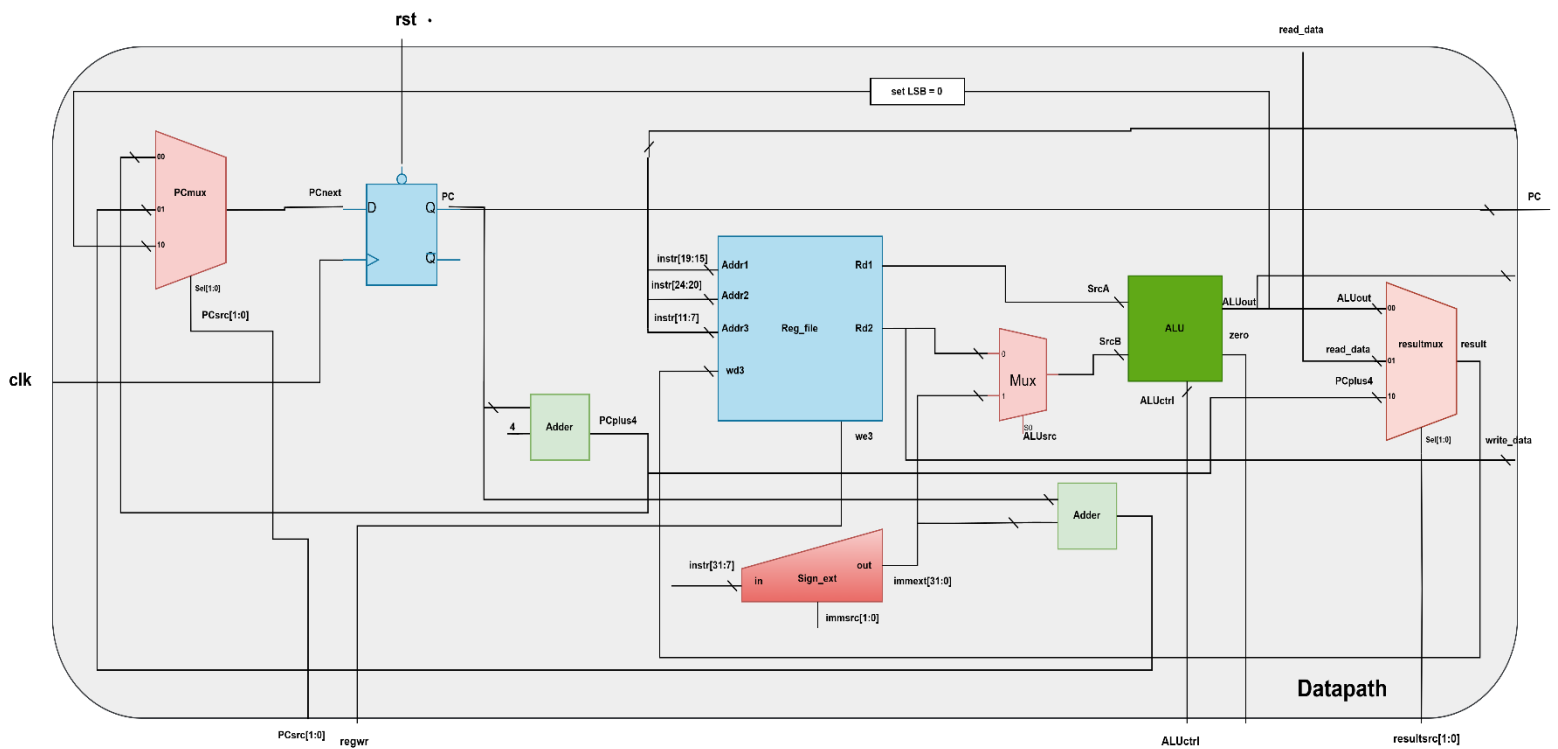

## 3. Design codes:

### 3.1 mux2x1

```
module mux2x1 #(parameter n = 32) (
  input wire sel      ,
  input wire [n-1:0] in0 , in1 ,
  output reg [n-1:0] out
);

always@(*)
begin
  if(sel)
    begin
      out = in1 ;
    end
  else
    begin
      out = in0 ;
    end
end

endmodule
```

### 3.2 mux3x1

```
module mux3x1 #(parameter n = 32) (
  input wire [1:0] sel      ,
  input wire [n-1:0] in0 , in1 , in2,
  output reg [n-1:0] out
);

always@(*)
begin
  if(sel == 2'b10 )
    begin
      out = in2 ;
    end
  else if (sel == 2'b01)
    begin
      out = in1 ;
    end
  else if (sel == 2'b00)
    begin
      out = in0 ;
    end
  else
    begin
      out = in0 ;
    end
end

endmodule
```

### 3.3 flip flop

```
module flip_flop #(parameter n = 32) (  
    input wire clk,  
    input wire rst,  
    input wire [n-1:0] d,  
    output reg [n-1:0] q  
);  
  
always@(posedge clk or posedge rst)  
begin  
    if(rst)  
        begin  
            q <= 0 ;  
        end  
    else  
        begin  
            q <= d ;  
        end  
    end  
end  
  
endmodule
```

### 3.4 adder

```
module adder (  
    input wire [31:0] in1,  
    input wire [31:0] in2,  
    output wire [31:0] out  
);  
  
assign out = in1 + in2 ;  
  
endmodule
```

### 3.5 sign extend

```
module Sign_ext (  
    input wire [31:7] in,  
    input wire [1:0] opcode,  
    output reg [31:0] out  
);  
  
always@(*)  
begin  
    case(opcode)  
        2'b00 : //I-type instruction  
            out = { {20{in[31]}} , in[31:20] } ;  
        2'b01 : //S-type instruction  
            out = { {20{in[31]}} , in[31:25] , in[11:7] } ;  
        2'b10 : //B-type instruction  
            out = { {20{in[31]}} , in[7] , in[31:25] , in[11:8] , 1'b0 } ;  
        2'b11 : //J-type instruction  
            out = { {12{in[31]}} , in[19:12] , in[20] , in[30:21] , 1'b0 } ;  
        default : out = 32'hxxxxxxxx ;  
    endcase  
end  
  
endmodule
```

## 3.6 reg file

```
module Reg_file (
input wire      clk,
input wire      rst,
input wire [4:0] Addr1,
input wire [4:0] Addr2,
input wire [4:0] Addr3,
input wire [31:0] wd3,
input wire      we3,
output reg [31:0] rd1,
output reg [31:0] rd2
);

reg [31:0] temp [0:31] ;
integer i ;
//clocked writing
always@(posedge clk or posedge rst)
begin
    if(rst)
        begin
            for(i=0 ; i < 16 ; i = i+1)
                begin
                    temp[i] <= 'h0 ;
                end
            end
        if(we3)
            begin
                temp[Addr3] <= wd3 ;
            end
        end

    //combinational reading
    always@(*)
    begin
        if(Addr1 == 0)
            begin
                rd1 = 0 ;
            end
        else
            begin
                rd1 = temp[Addr1] ;
            end

        if(Addr2 == 0)
            begin
                rd2 = 0 ;
            end
        else
            begin
                rd2 = temp[Addr2] ;
            end
    end

endmodule
```

### 3.7 ALU

```
module Alu (
input wire [1:0] ALUctrl ,
input wire [31:0] A , B ,
output reg [31:0] ALUout,
output wire      zero
);

assign zero = (ALUout == 0)? 1 : 0 ;

always@(*)
begin
    case(ALUctrl)
        2'b00: ALUout = A + B ;
        2'b01: ALUout = A - B ;
        2'b10: ALUout = A & B ;
        2'b11: ALUout = A | B ;
        default: ALUout = 0 ;
    endcase
end

endmodule
```

### 3.8 ALU decoder

```
module Alu_decoder (
input wire [1:0]  ALUop,
input wire [2:0]  funct3,
input wire        funct7_5,
input wire        op_5,
output reg [1:0] ALUctrl
);

always@(*)
begin
    case(ALUop)
        2'b00 : ALUctrl = 2'b00 ; //adding for lw,sw,jalr
        2'b01 : ALUctrl = 2'b01 ; //subtracting for beq,bne
        2'b10 : //R,I-type instructions
        begin
            case(funct3)
                3'b000 :
                    begin
                        if({op_5,funct7_5} == 3'b11)
                            begin
                                ALUctrl = 2'b01 ; //subtraction for sub
                            end
                        else
                            begin
                                ALUctrl = 2'b00 ; //adding for add,addi
                            end
                        end
                    3'b111 : ALUctrl = 2'b10 ; //anding for and,andi
                    3'b110 : ALUctrl = 2'b11 ; //oring for or,ori
                    default : ALUctrl = 2'bxx ;
                endcase
            end
        default : ALUctrl = 2'bxx ;
    endcase
end

endmodule
```

### 3.9 main decoder

```
module main_decoder (
input wire [6:0] op,
output reg      jump,
output reg      jalr,
output reg      branch,
output reg [1:0] immsrc,
output reg      ALUsrc,
output reg [1:0] ALUop,
output reg [1:0] resultsrc,
output reg      regwr,
output reg      memwr
);
always@(*)
begin
    case(op)
        7'b0000011 : //lw instruction
        begin
            regwr      = 1'b1 ;
            immsrc      = 2'b00 ;
            ALUsrc      = 1'b1 ;
            memwr       = 1'b0 ;
            resultsrc   = 2'b01 ;
            branch      = 1'b0 ;
            ALUop       = 2'b00 ;
            jump        = 1'b0 ;
            jalr        = 1'b0 ;
        end
        7'b0100011 : //sw instruction
        begin
            regwr      = 1'b0 ;
            immsrc      = 2'b01 ;
            ALUsrc      = 1'b1 ;
            memwr       = 1'b1 ;
            resultsrc   = 2'bxx ;
            branch      = 1'b0 ;
            ALUop       = 2'b00 ;
            jump        = 1'b0 ;
            jalr        = 1'b0 ;
        end
        7'b0110011 : //R-type instruction
        begin
            regwr      = 1'b1 ;
            immsrc      = 2'bxx ;
            ALUsrc      = 1'b0 ;
            memwr       = 1'b0 ;
            resultsrc   = 2'b00 ;
            branch      = 1'b0 ;
            ALUop       = 2'b10 ;
            jump        = 1'b0 ;
            jalr        = 1'b0 ;
        end
        7'b1100011 : //beq instruction
        begin
            regwr      = 1'b0 ;
            immsrc      = 2'b10 ;
            ALUsrc      = 1'b0 ;
            memwr       = 1'b0 ;
            resultsrc   = 2'bxx ;
            branch      = 1'b1 ;
            ALUop       = 2'b01 ;
            jump        = 1'b0 ;
            jalr        = 1'b0 ;
        end
    end
end
```



```

7'b0010011 : //I-type instruction (except jalr)
begin
    regwr      = 1'b1 ;
    immsrc     = 2'b00 ;
    ALUsrc     = 1'b1 ;
    memwr      = 1'b0 ;
    resultsrc  = 2'b00 ;
    branch     = 1'b0 ;
    ALUop      = 2'b10 ;
    jump       = 1'b0 ;
    jalr       = 1'b0 ;
end
7'b1101111 : //jal instruction
begin
    regwr      = 1'b1 ;
    immsrc     = 2'b11 ;
    ALUsrc     = 1'bx ;
    memwr      = 1'b0 ;
    resultsrc  = 2'b10 ;
    branch     = 1'b0 ;
    ALUop      = 2'bx ;
    jump       = 1'b1 ;
    jalr       = 1'b0 ;
end
7'b1100111 : //jalr instruction
begin
    regwr      = 1'b1 ;
    immsrc     = 2'b00 ;
    ALUsrc     = 1'b1 ;
    memwr      = 1'b0 ;
    resultsrc  = 2'b10 ;
    branch     = 1'b0 ;
    ALUop      = 2'b00 ;
    jump       = 1'b0 ;
    jalr       = 1'b1 ;
end
default :
begin
    regwr      = 1'bx ;
    immsrc     = 2'bx ;
    ALUsrc     = 1'bx ;
    memwr      = 1'bx ;
    resultsrc  = 2'bx ;
    branch     = 1'bx ;
    ALUop      = 2'bx ;
    jump       = 1'bx ;
    jalr       = 1'bx ;
end
endcase
end

endmodule

```

### 3.10 data\_path

```
module datapath (
  //global inputs
  input wire clk,
  input wire rst,
  //instr memory inputs
  input wire [31:0] instr,
  //data memory inputs
  input wire [31:0] read_data,
  //CU inputs
  input wire [1:0] PCsrc,
  input wire [1:0] immsrc,
  input wire      ALUsrc,
  input wire [1:0] ALUctrl,
  input wire [1:0] resultsrc,
  input wire      regwr,
  //instr memory outputs
  output wire [31:0] PC,
  //data memory outputs
  output wire      zero,
  output wire [31:0] ALUout,
  output wire [31:0] write_data
);

wire [31:0] PCnext , PCplus4 , PCtarget ;
wire [31:0] result ;
wire [31:0] SrcA , SrcB ;
wire [31:0] immext ;

flip_flop #(32) u_ff(
  .clk(clk),
  .rst(rst),
  .d(PCnext),
  .q(PC)
);
mux3x1 #(32) u_pcmux (
  .sel(PCsrc) ,
  .in0(PCplus4) ,
  .in1(PCtarget) ,
  .in2( {ALUout[31:1],1'b0} ),
  .out(PCnext)
);

Reg_file u_regf (
  .clk(clk),
  .rst(rst),
  .Addr1(instr[19:15]),
  .Addr2(instr[24:20]),
  .Addr3(instr[11:7]),
  .wd3(result),
  .we3(regwr),
  .rd1(SrcA),
  .rd2(write_data)
);

Sign_ext u_signext(
  .in(instr[31:7]),
  .opcode(immsrc),
  .out(immext)
);
```

```

mux2x1 #(32) u_alumux (
  .sel(ALUsrc) ,
  .in0(write_data) ,
  .in1(immext) ,
  .out(SrcB)
);

adder u_adderplus4 (
  .in1(PC),
  .in2(32'd4),
  .out(PCplus4)
);

adder u_addertarget (
  .in1(PC),
  .in2(immext),
  .out(PCtarget)
);

Alu u_ALU (
  .ALUctrl(ALUctrl) ,
  .A(SrcA) ,
  .B(SrcB) ,
  .ALUout(ALUout) ,
  .zero(zero)
);

mux3x1 #(32) u_resultmux (
  .sel(resultsrc) ,
  .in0(ALUout) ,
  .in1(read_data) ,
  .in2(PCplus4),
  .out(result)
);

endmodule

```

### 3.11 control\_unit

```

module control_unit(
  //instr memory inputs
  input wire [6:0] op,
  input wire [2:0] funct3,
  input wire      funct7_5,
  //Alu inputs
  input wire      zero,
  //datapath outputs
  output wire [1:0] PCsrc,
  output wire [1:0] immsrc,
  output wire      ALUsrc,
  output wire [1:0] ALUctrl,
  output wire [1:0] resultsrc,
  output wire      regwr,
  //data memory output
  output wire      memwr
);

wire [1:0] ALUop ;
wire      jump;
wire      jalr;
wire      branch;
wire      zero_new ;

assign zero_new = (funct3[0] && op == 7'b1100011)? !zero : zero ;

assign PCsrc = {jalr, ((zero_new & branch) | jump) } ;

```

```

main_decoder u_md (
    .op(op),
    .jump(jump),
    .jalr(jalr),
    .branch(branch),
    .immsrc(immsrc),
    .ALUsrc(ALUsrc),
    .ALUop(ALUop), //
    .resultsrc(resultsrc),
    .regwr(regwr),
    .memwr(memwr)
);

Alu_decoder u_ad (
    .ALUop(ALUop),
    .funct3(funct3),
    .funct7_5(funct7_5),
    .op_5(op[5]),
    .ALUctrl(ALUctrl)
);

endmodule

```

### 3.12 top\_RISCV

```

module top_RISCV #(parameter n = 10 , m = 32) (
    input wire clk,
    input wire rst,
    output wire [n-1:0] addr,
    output wire [m-1:0] write_data,
    output wire      memwr,
    output wire [31:0] read_data,
    output wire [31:0] PC,
    output wire [31:0] instr
);

    wire [1:0] PCsrc ;
    wire [1:0] immsrc ;
    wire      ALUsrc ;
    wire [1:0] ALUctrl ;
    wire [1:0] resultsrc ;
    wire      regwr ;
    wire      zero ;
    wire [31:0] ALUout ;

    assign addr = ALUout[9:0] ;

    datapath u_dp (
        .clk(clk),
        .rst(rst),
        //instr memory inputs
        .instr(instr),
        //data memory inputs
        .read_data(read_data),
        //CU inputs
        .PCsrc(PCsrc),
        .immsrc(immsrc),
        .ALUsrc(ALUsrc),
        .ALUctrl(ALUctrl),
        .resultsrc(resultsrc),
        .regwr(regwr),
        //instr memory outputs
        .PC(PC),
        //data memory outputs
        .zero(zero),
        .ALUout(ALUout),
        .write_data(write_data)
    );

```

```

control_unit u_cu (
.op(instr[6:0]),
.funct3(instr[14:12]),
.funct7_5(instr[30]),
//Alu inputs
.zero(zero),
//datapath outputs
.PCsrc(PCsrc),
.immsrc(immsrc),
.ALUsrc(ALUsrc),
.ALUctrl(ALUctrl),
.resultsrc(resultsrc),
.regwr(regwr),
//data memory output
.memwr(memwr)
);

endmodule

```

### 3.13 instr\_rom

```

module instr_rom #(parameter n = 10 , m = 32 ) (
input wire [n-1:0] addr,
output wire [m-1:0] read_data
);

reg [m-1:0] mem [0:2**(n-2)-1] ; //n-2 for word addressable memory

initial
begin
$readmemh("testcases.txt", mem);
end

assign read_data = mem[addr[n-1:2]] ; //[n-1:2] for word addressable memory

endmodule

```

### 3.14 data\_ram

```

module data_ram #(parameter n = 10 , m = 32 ) (
input wire clk,
input wire rst,
input wire we,
input wire [n-1:0] addr,
input wire [m-1:0] write_data,
output wire [m-1:0] read_data
);

reg [7:0] mem [0:1023] ; //n-2 for word addressable memory
integer i ;

always@(posedge clk or posedge rst)
begin
if(rst)
begin
for(i=0 ; i < 2**(n-2) ; i = i+1)
begin
mem[i] <= 'h0 ;
end
end
end

```

```

    else if(we)
    begin
        mem[addr[n-1:2]] <= write_data ; //[n-1:2] for word addressable memory
    end
end

assign read_data = mem[addr[n-1:2]] ; //[n-1:2] for word addressable memory

endmodule

```

## 4.simulation

### 4.1 top\_RISCV\_tb

```

`timescale 1ps/1fs
module top_RISCV_tb #(parameter n = 10 , m = 32) ();

reg clk ;
reg rst ;
wire [n-1:0] addr;
wire [m-1:0] write_data;
wire      memwr ;
wire [31:0] read_data;
wire [31:0] PC;
wire [31:0] instr;

//instantiation
top_RISCV #(10,32) u_top (
.clk(clk),
.rst(rst),
.addr(addr),
.write_data(write_data),
.memwr(memwr),
.read_data(read_data),
.PC(PC),
.instr(instr)
);

instr_rom #(10,32) u_ins_rom (
.addr(PC[9:0]),
.read_data(instr)
);

data_ram #(10,32) u_data_ram (
.clk(clk),
.rst(rst),
.we(memwr),
.addr(addr),
.write_data(write_data),
.read_data(read_data)
);

initial
begin
    clk = 0 ;
    forever #500 clk = ~clk ;
end

initial
begin
    rst = 1'b1 ;
    #1000
    rst = 1'b0 ;
end

```

```

always@(negedge clk)
begin
    if(memwr)
        begin
            if(write_data == 2 && addr == 96)
                begin
                    $display("time = %0t , write_data = %4d ,   addr = %8d ,testcase1 passed (first sw)",
$time , write_data , addr) ;
                end
            else if(write_data == 4 && addr == 92)
                begin
                    $display("time = %0t , write_data = %4d ,   addr = %8d ,testcase2 passed (second sw)",
$time , write_data , addr) ;
                    $stop ;
                end
            else
                begin
                    $display("time = %0t , write_data = %4d ,   addr = %8d ,testcase1,2 faild", $time ,
write_data , addr) ;
                    $stop ;
                end
            end
        end
    end
endmodule

```

## 4.2 assembly code and its output

main: addi x2, x0, 5	# x2 = 5 0 00500113
addi x3, x0, 12	# x3 = 12 4 00C00193
addi x7, x3, -9	# x7 = (12 - 9) = 3 8 FF718393
or x4, x7, x2	# x4 = (3 OR 5) = 7 C 0023E233
and x5, x3, x4	# x5 = (12 AND 7) = 4 10 0041F2B3
add x5, x5, x4	# x5 = 4 + 7 = 11 14 004282B3
beq x5, x7, end	# shouldn't be taken 18 02728463
beq x4, x0, around	# shouldn't be taken 1C 00020463
addi x5, x0, 0	# x5 = 0 + 0 = 0 20 00000293
around: add x7, x4, x5	# x7 = (7 + 0) = 7 24 005203B3
sub x7, x7, x2	# x7 = (7 - 5) = 2 28 402383B3
sw x7, 84(x3)	# <b>[96] = 2</b> 2C 0471AA23 (testcase1)
lw x2, 96(x0)	# x2 = [96] = 2 30 06002103

add x9, x2, x5                   #  $x9 = (2 + 0) = 2$  34 005104B3  
 jal x3, end                    # jump to end, x3 = 0x3C 38 008001EF  
 addi x2, x0, 1                # shouldn't execute 3C 00100113  
 end: add x2, x2, x9            #  $x2 = (2 + 2) = 4$  40  
 sw x2, 0x20(x3)               # **[92]** = **4** 44 0221A023 (testcase2)  
 done: beq x2, x2, done        # infinite loop 48 00210063


testcases.txt content

```

00500113
00C00193
FF718393
0023E233
0041F2B3
004282B3
02728463
00020463
00000293
005203B3
402383B3
0471AA23
06002103
005104B3
008001EF
00100113
00910133
0221A023
00210063
  
```



## 4.3 simulation results

 

mem[23]\_word addressable = mem[23\*4] = mem[92]

mem[24]\_word addressable = mem[24\*4] = mem[96]\_word addressable

```
VSIM 11> run -all
# time = 12000000 , write_data = 2 , addr = 96 ,testcase1 passed (first sw)
# time = 17000000 , write_data = 4 , addr = 92 ,testcase2 passed (second sw)
```